



COMSATS University Islamabad, Lahore Campus
Department of Electrical and Computer Engineering

Assignment 2– SPRING 2026

Course Title:	Fundamentals of Digital Logic Design	Course Code:	EEE240	Credit Hours:	3(2,1)
Course Instructor:	Dr. Ali Raza	Programme Name:	BSE		
Semester:	3rd	SP25	Section:	A	Date:
Submission Date:	14 th April, 2025			Maximum Marks:	40
Name:				Registration Number:	

Important Instructions / Guidelines:

- In case of plagiarism, you will be marked ZERO.

Problem 1:

Apply gate minimization technique using 4-variable K-map to simplify the following Boolean expression:

$$\bar{A}\bar{B}\bar{C}\bar{D} + A\bar{C}\bar{D} + \bar{B}C\bar{D} + \bar{A}BCD + B\bar{C}D$$

Problem 2:


Analyze the following Boolean function F , together with the don't-care conditions d , to express function in sum-of-minterms form:

$$F(A, B, C, D) = (0, 6, 8, 13, 14)$$

$$d(A, B, C, D) = (2, 4, 10)$$

Problem 3:

Using digital circuit analysis technique, evaluate the Boolean expression for output F and G in terms of the input variables A, B, C and D . Then use K-map to simplify the expression.

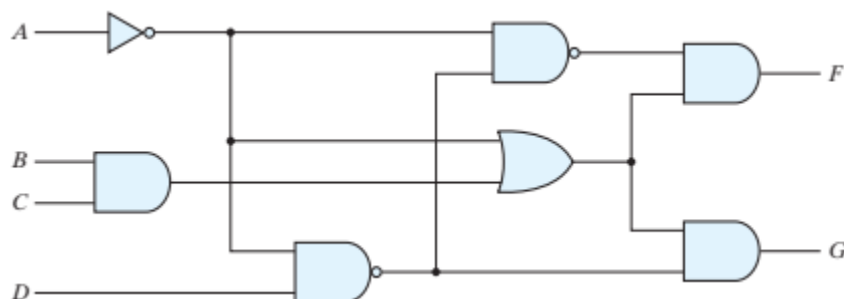

Problem 4:

Design a 4-bit combinational circuit that generates the 2's complement of a 4-bit binary input number. Provide the truth table, Karnaugh map (K-map), and the resulting circuit diagram in your working.