



COMSATS University Islamabad, Lahore Campus
Department of Electrical and Computer Engineering

Assignment 2 - SPRING 2026

Course Title:	Fundamentals of Digital Logic Design			Course Code:	EEE240	Credit Hours:	3(2,1)
Course Instructor:	Dr. Ali Raza			Programme Name:	BSE		
Semester:	3rd		SP25	Section:	A	Date:	12-05-26
Submission Date:	14 th April, 2025				Maximum Marks:	40	
Name:	M. Athar Abbas				Registration Number:	SP25-BSE-	
<u>Important Instructions / Guidelines:</u>							
• In case of plagiarism, you will be marked ZERO.							

Problem 1:

Apply gate minimization technique using 4-variable K-map to simplify the following Boolean expression:

$$\overline{A}\overline{B}\overline{C}\overline{D} + A\overline{C}\overline{D} + \overline{B}\overline{C}\overline{D} + \overline{A}BC\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}D + \overline{B}\overline{C}DA + \overline{B}\overline{C}DA \quad (\text{Standard SOP})$$

Simplified expression: $\overline{A}BD + A\overline{B}\overline{C} + \overline{B}\overline{D}$ (K-map on back page)

Problem 2:


Analyze the following Boolean function F, together with the don't-care conditions d, to express function in sum-of-minterms form:

$$F(A, B, C, D) = (0, 6, 8, 13, 14) \\ d(A, B, C, D) = (2, 4, 10)$$

Simplified expression: $\overline{B}\overline{D} + C\overline{D} + A\overline{B}C\overline{D}$


Problem 3:

Using digital circuit analysis technique, evaluate the Boolean expression for output F and G in terms of the input variables A, B, C and D. Then use K-map to simplify the expression.

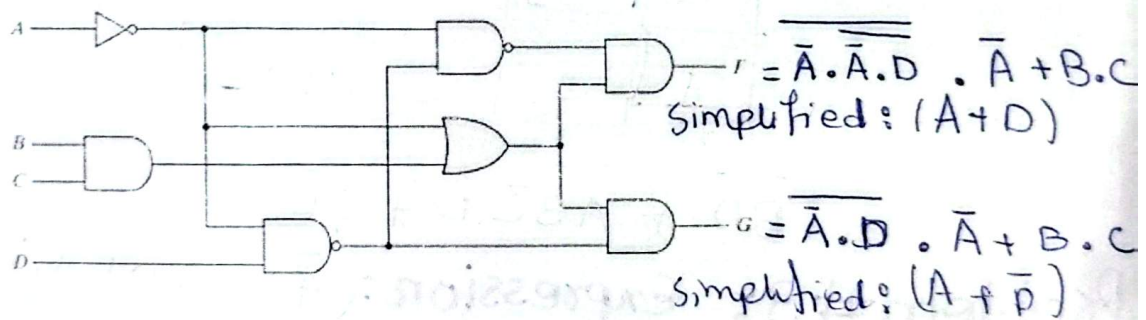

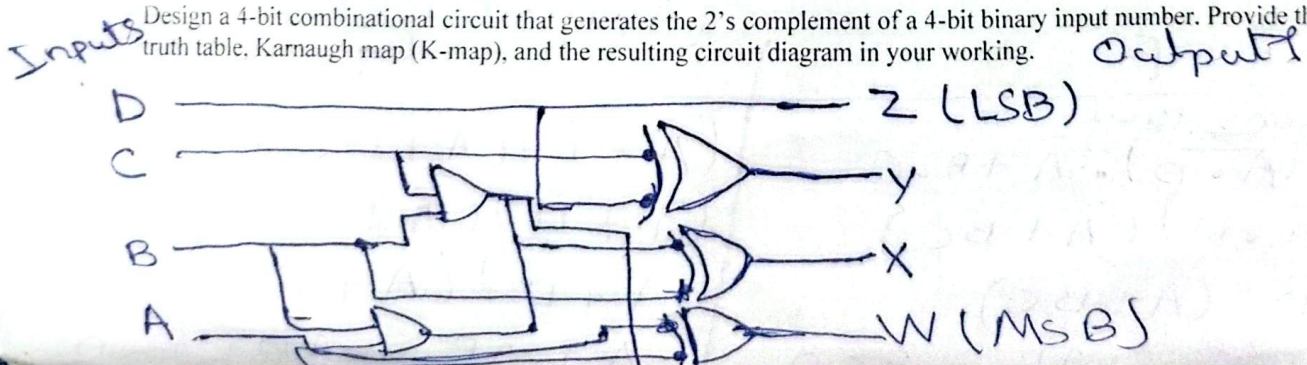Problem 4:

Design a 4-bit combinational circuit that generates the 2's complement of a 4-bit binary input number. Provide the truth table, Karnaugh map (K-map), and the resulting circuit diagram in your working.



Problem #1: CD Kmap: $F = \Sigma($

		00	01	11	10
00		1	0	0	1
01		0	1	1	0
11		1	1	0	0
10		1	0	0	1

$$= \bar{A}BD + AB\bar{C} + \bar{B}\bar{D}$$

Problem #2: Kmap CD

		00	01	11	10
00		1	0	0	X
01		X	0	0	1
11		0	1	0	1
10		1	0	0	X

$$= \bar{B}\bar{D} + AB\bar{C}D + C\bar{D}$$

Problem #3: Expression: $(\bar{A} \cdot (\bar{A} \cdot D))(\bar{A} + B \cdot C) = F$

$$(\bar{A} \cdot D)(\bar{A} + B \cdot C) = G$$

de Morgan's law:

$$(\bar{A}) + (\bar{A} \cdot D) \cdot \bar{A} + B \cdot C$$

$$(A + \bar{A} \cdot D)(\bar{A} + BC)$$

$$(A + D)(\bar{A} + BC)$$

$$A + ABC + \bar{A}D + BCD$$

$$(\bar{A} + \bar{D})(\bar{A} + BC)$$

$$(A + \bar{D})(\bar{A} + BC)$$

$$(A + \bar{D})(A + BC)$$

$$A + A\bar{D} + A\bar{D} + BCD$$

K-map:

F

	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	1	1	1	1
10	1	1	1	1

$$F = (A + D)$$

G

	00	01	11	10
00	1	0	0	0
01	1	0	0	0
11	1	1	1	1
10	1	1	1	1

$$G = (A + \bar{D})$$

Q4) Kmap for output Y:

	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

Kmap for output Z:

	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

$$Y = C \oplus D$$

$$Z = D$$

Now

$$W = A \oplus (B + C + D)$$

$$X = B \oplus C + D$$

$$Y = C \oplus D$$

$$Z = D$$

Binary				1's complement	Adding 1	2's complement			
A	B	C	D						
0	0	0	0	1111	+ 1	0000	0	0	0
0	0	0	1	1110	+ 1	1111	1	1	1
0	0	1	0	1101	+ 1	1110	1	1	1
0	0	1	1	1100	+ 1	1101	1	1	0
0	1	0	0	1011	+ 1	1010	1	0	0
0	1	0	1	1010	+ 1	1001	1	0	1
0	1	1	0	1001	+ 1	1000	1	0	0
0	1	1	1	1000	+ 1	0111	0	1	1
1	0	0	0	0111	+ 1	0110	0	1	1
1	0	0	1	0110	+ 1	0101	0	1	0
1	0	1	0	0101	+ 1	0100	0	1	0
1	0	1	1	0100	+ 1	0011	0	0	1
1	1	0	0	0011	+ 1	0010	0	0	1
1	1	0	1	0010	+ 1	0001	0	0	0
1	1	1	0	0001	+ 1	0000	0	0	0
1	1	1	1	0000	+ 1	1111	1	1	1

K-map for output Bit W (MSB)

		00	01	10	11
AB	00	0	1	1	1
	01	1	1	1	1
	11	0	0	0	0
	10	1	0	0	0

$$W = A \oplus (B + C + D)$$

K-Map for output X

		00	01	10	11
AB	00	0	1	1	1
	01	1	0	0	0
	11	1	0	0	0
	10	0	1	1	1

$$X = B \oplus C + D$$