

Day: _____

Assignment # 3:

Date: _____

M. Athar Abbas

SP25-BSE-082

F. DLD

1) Flip-flop equations: -

F-F

J

K

A(top)

$$J \cdot A = X \cdot B$$

$$K \cdot A = X'$$

B(bottom)

$$J \cdot B = X + A$$

$$K \cdot B = X'$$

2) State Equations:

using JK characteristic equation:

$$Q(t+1) = J \cdot Q' + K' \cdot Q$$

For F-F A:

$$A(t+1) = J \cdot A \cdot A' + K' \cdot A \cdot A =$$

$$X \cdot B \cdot A' = X \cdot A = X(A+B)$$

For F-F B:

$$B(t+1) = J \cdot B \cdot B' + K' \cdot B \cdot B = (X + A) \cdot B'$$

$$+ X \cdot B = X \neq A \cdot B'$$

3) Output Equation:

$$Y = A \cdot B = Q_1 \cdot Q_2$$


4) State Table

Page: _____

Date: _____

Present State (A,B)	Input X	A^+, B^+	Y
0,0	0	0,0	0
0,0	1	0,1	0
0,1	0	0,0	0
0,1	1	1,1	0
1,0	0	0,1	0
1,0	1	1,1	0
1,1	0	0,0	1
1,1	1	1,1	1

5) state Diagram:

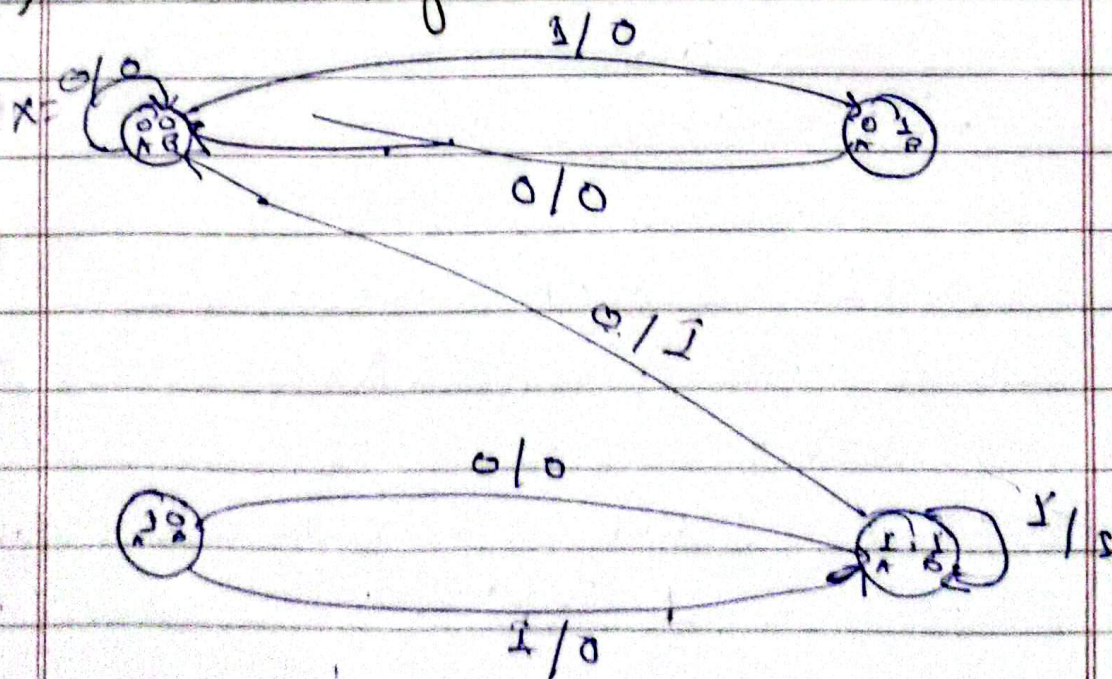

$Y=1$ transitions (A=B=1)